
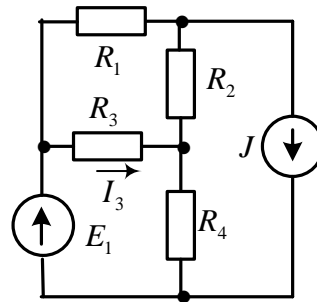


Exemplo Teorema de Thevenin


Calcular a corrente assinalada no circuito dado utilizando o Teorema de Thevenin.

$$E_1 = 100 \text{ V} ; J = 6 \text{ A} ; R_1 = 2,5 \Omega$$
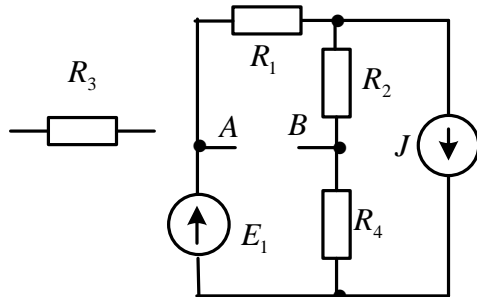
$$R_2 = 10 \Omega ; R_3 = 40 \Omega ; R_4 = 20 \Omega$$


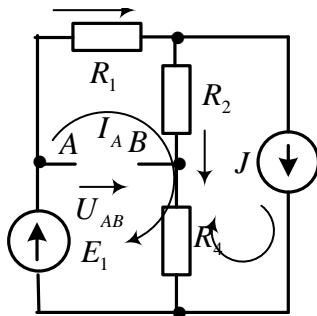
$$U_{AB} - I_2 R_2 - I_1 R_1 = 0 \rightarrow U_{AB} = I_2 R_2 + I_1 R_1 = 47,75 \text{ V}$$



$$I_A (R_1 + R_2 + R_4) - J (R_2 + R_4) = E_1 \rightarrow$$

$$I_A = \frac{E_1 + J (R_2 + R_4)}{R_1 + R_2 + R_4} = 8,62 \text{ A}$$

$$I_1 = I_A ; I_2 = I_A - J = 2,62 \text{ A}$$

$$R_{AB} = \frac{R_4 (R_1 + R_2)}{R_4 + (R_1 + R_2)} = 7,69 \Omega$$

$$E_1 = 100 \text{ V} ; J = 6 \text{ A} ; R_1 = 2,5 \Omega$$

$$R_2 = 10 \Omega ; R_3 = 40 \Omega ; R_4 = 20 \Omega$$

$$I_3 = \frac{U_{AB}}{R_{AB} + R_3} = 1 \text{ A}$$

