

TEORIA DE CIRCUITOS 2023

Exemplos de corrente alternada

1. Transformar:

a) $i = 1,414 \operatorname{sen}(\omega t + 15) A$ complexa

$$a) \bar{I}_m = 1,414 \angle 15^\circ A$$

$$\bar{I} = 1 \angle 15^\circ A$$

b) $\bar{U} = 44 \cdot \sqrt{2} \angle -45^\circ V$ instantânea

$$u = 88 \sin(\omega t - 45^\circ) V$$

2. $i_1 = 7,07 \operatorname{sen}(\omega t + 15) A$; $i_2 = 10,12 \operatorname{sen}(\omega t + 45) A$

Calcular $i = i_1 + i_2 =$

$$\bar{I}_{1m} = 7,07 \angle 15^\circ A = (7,07 \cos 15 + j 7,07 \operatorname{sen} 15) = (6,82 + j 1,82) A;$$

$$\bar{I}_{2m} = 10,12 \angle 45^\circ A = 10,12 \cos 45 + j 10,12 \operatorname{sen} 45 = (7,15 + j 7,15) A$$

$$\bar{I}_m = (13,97 + j 8,97) = 16,60 \angle 32,7^\circ A$$

$$i = 16,60 \operatorname{sen}(\omega t + 32,7^\circ) A$$

3. $u = 127 \operatorname{sen}(\omega t + 15) V$; $i = 12,15 \operatorname{sen}(\omega t - 15) A$

Calcular $Z =$

$$\bar{Z} = \frac{\bar{U}}{\bar{I}} = 10,45 \angle 30^\circ \Omega = (9,04 + j 5,22) \Omega$$

$$\bar{U} = 89,8 \angle 15^\circ V; \bar{I} = 8,59 \angle -15^\circ A$$

4. Calcular a impedância equivalente e as correntes do circuito abaixo.

$$R_1 = 2\Omega, R_2 = 3\Omega; L_2 = 12,732 \text{ mH}, L_3 = 9,549 \text{ mH}$$

$$f = 50 \text{ Hz}; C_3 = 127 \mu\text{F}; u_{ab} = 12 \text{ sen}(\omega t + 35^\circ), \text{ V}$$

$$X_2 = \omega L_2 = 2\pi f L_2 = 4\Omega$$

$$X_3 = \omega L_3 = 2\pi f L_3 = 3\Omega$$

$$X_{C3} = \frac{1}{\omega C_3} = \frac{1}{2\pi f C_3} = 25,06\Omega$$

$$\bar{Z}_{EQ} = R_1 + \frac{(R_2 + jX_2)j(X_3 - X_{C3})}{R_2 + j(X_3 + X_2 - X_{C3})} = 7,6\angle 33,22^\circ\Omega$$

$$\bar{U}_{ab} = 8,49\angle 35^\circ \text{ V}$$

$$\bar{I}_1 = \frac{\bar{U}_{ab}}{\bar{Z}_{EQ}} = 1,12\angle 1,78^\circ \text{ A}; \bar{I}_3 = \bar{I}_1 \frac{R_2 + jX_2}{R_2 + j(X_3 + X_2 - X_{C3})} = 0,31\angle 135,5^\circ \text{ A}$$

$$\bar{I}_2 = \bar{I}_1 - \bar{I}_3 = 1,35\angle -7,75^\circ \text{ A}$$

$$\bar{S}_{FOR} = \bar{U}_{ab} \bar{I}_1^* = 8,49\angle 35^\circ \cdot 1,12\angle -1,78^\circ = (7,95 + j5,21) \text{ VA}$$

$$P_{CONS} = I_1^2 R_1 + I_2^2 R_2 = (1,12)^2 \cdot 2 + (1,35)^2 \cdot 3 = 7,97 \text{ W}$$

$$Q_{CONS} = I_3^2 (X_3 - X_{C3}) + I_2^2 X_2 = (0,31)^2 (3 - 25,06) + (1,35)^2 \cdot 4 = 5,17 \text{ VAR}$$

